

# Gajendra Processor

Lab Report

submitted by

Aasritha Yadav C (CS22B064), K. A. Vignesh (CS22B076)

Under the supervision

of

Dr.Ayon Chakraborty



Computer Science and Engineering

Indian Institute of Technology Madras

Jul - Nov 2023

# Contents

<b>1</b>	<b>General CPU Register</b>	<b>5</b>
1.1	Diagram . . . . .	5
1.2	I/O Control . . . . .	5
1.3	Working . . . . .	5
<b>2</b>	<b>Program Counter</b>	<b>6</b>
2.1	Diagram . . . . .	6
2.2	Working . . . . .	6
2.3	PC_INC . . . . .	6
2.4	PC_OUT . . . . .	6
2.5	PC_LOAD . . . . .	6
<b>3</b>	<b>MEMORY</b>	<b>7</b>
3.1	Diagram . . . . .	7
3.2	MEM_OUT . . . . .	7
<b>4</b>	<b>MEMORY ADDRESS REGISTER</b>	<b>8</b>
4.1	Diagram . . . . .	8
4.2	MAR_IN . . . . .	8
<b>5</b>	<b>INSTRUCTION REGISTER</b>	<b>9</b>
5.1	Diagram . . . . .	9
5.2	INS_REG_IN . . . . .	9
5.3	INS_REG_OUT . . . . .	9
5.4	CTRL . . . . .	9
<b>6</b>	<b>INSTRUCTION DECODER</b>	<b>10</b>
6.1	Diagram . . . . .	10
6.2	INS_DEC_OUT . . . . .	10
6.3	ALU_OUT . . . . .	10
<b>7</b>	<b>Arithmetic and Logic Unit(ALU)</b>	<b>11</b>
7.1	ADD . . . . .	11
7.2	SUB . . . . .	11
<b>8</b>	<b>Status Register</b>	<b>12</b>
8.1	Diagram . . . . .	12
8.2	I/O . . . . .	12
8.3	Uses . . . . .	12
<b>9</b>	<b>Control Processor</b>	<b>13</b>
9.1	Diagram . . . . .	13
9.2	I/O . . . . .	13
9.3	Working . . . . .	13
9.4	Ring Counter . . . . .	13
9.5	EEPROM Programming . . . . .	13

<b>10 Micro instructions and Controller Logic Design</b>	<b>14</b>
10.1 <b>NOP</b> : . . . . .	14
10.2 <b>LDA</b> : . . . . .	14
10.3 <b>ADD</b> : . . . . .	14
10.4 <b>SUB</b> : . . . . .	15
10.5 <b>LDI</b> : . . . . .	15
10.6 <b>JNZ</b> : . . . . .	15

## List of Figures

1	8-bit Register . . . . .	5
2	Program Counter . . . . .	6
3	Memory . . . . .	7
4	Memory Address Register . . . . .	8
5	Instruction Register . . . . .	9
6	Instruction Decoder . . . . .	10
7	Gajendra ALU . . . . .	11
8	Status Register . . . . .	12
9	Control Processor . . . . .	13
10	Micro Instruction for NOP . . . . .	14
11	Micro instruction for LDA . . . . .	14
12	Micro instruction for ADD . . . . .	14
13	Micro instruction for SUB . . . . .	15
14	Micro instruction for LDI . . . . .	15
15	Micro instruction for JNZ . . . . .	15

# 1 General CPU Register

## 1.1 Diagram

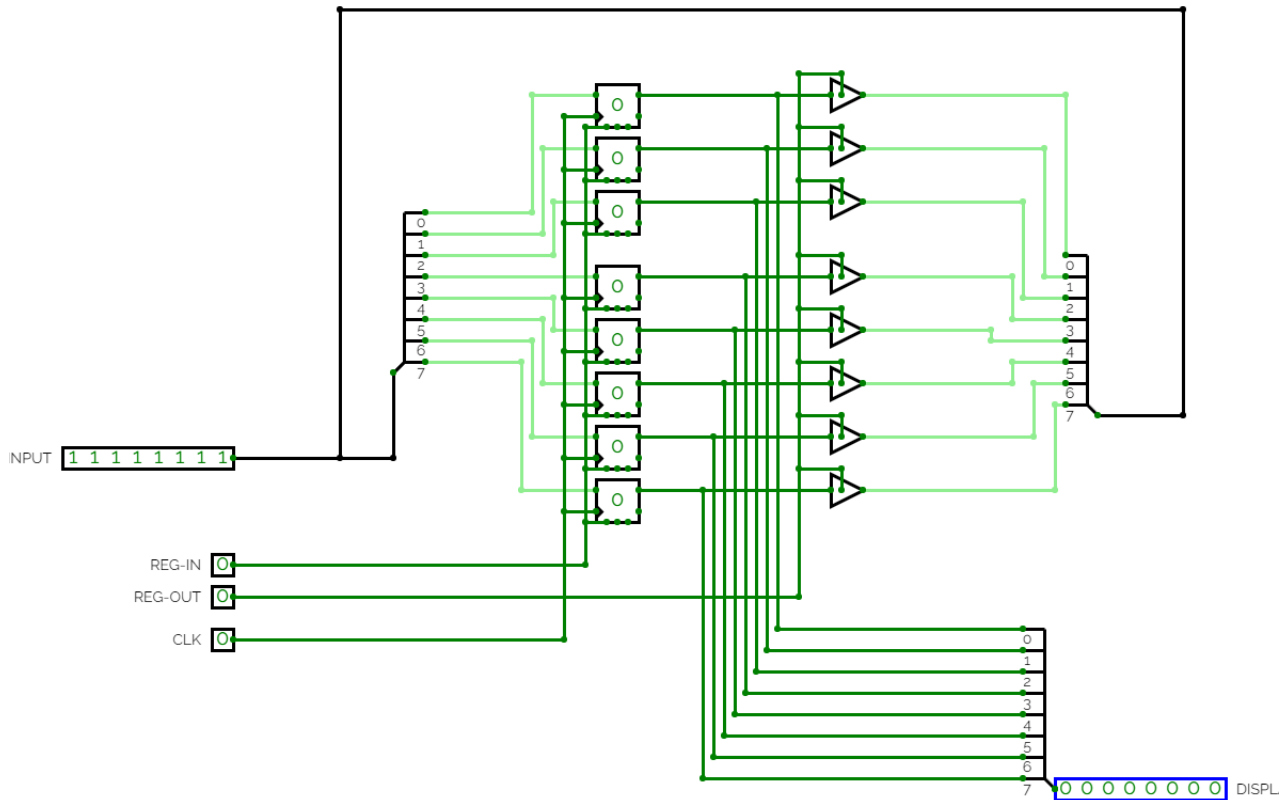


Figure 1: 8-bit Register

## 1.2 I/O Control

The register consists of a bidirectional common 'I/O' line which stores the 8 bit input from common bus. The 8 bit value can later be sent to output. The flow of data is controlled by the signals REG\_in and REG\_out.

## 1.3 Working

The register consists of D flip flops, responsible for the storage of memory. REG\_act as the control signal for input, when it is 1 the input is read from the common bus while REG\_out is the control signal for output in the same way.



## 3 MEMORY

### 3.1 Diagram

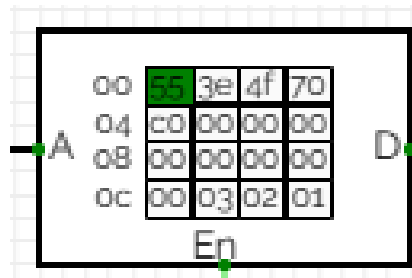


Figure 3: Memory

Memory is the ROM which contains both instruction and data required for a program. The following are the functionalities that are present in the Memory.

### 3.2 MEM\_OUT

The ROM's output is controlled by a tri-state buffer. MEM\_OUT acts as the enable line for this tri-state buffer. If MEM\_OUT = 1 then the memory outputs a 8-bit output into the common bus.

## 4 MEMORY ADDRESS REGISTER

During a computer run , the 4-bit address in the Programming Counter is latched into the MAR .Then the MAR applies this 4-bit address to the Memory where a read operation is performed.

The following are the functionalities that are present in the MAR .

### 4.1 Diagram

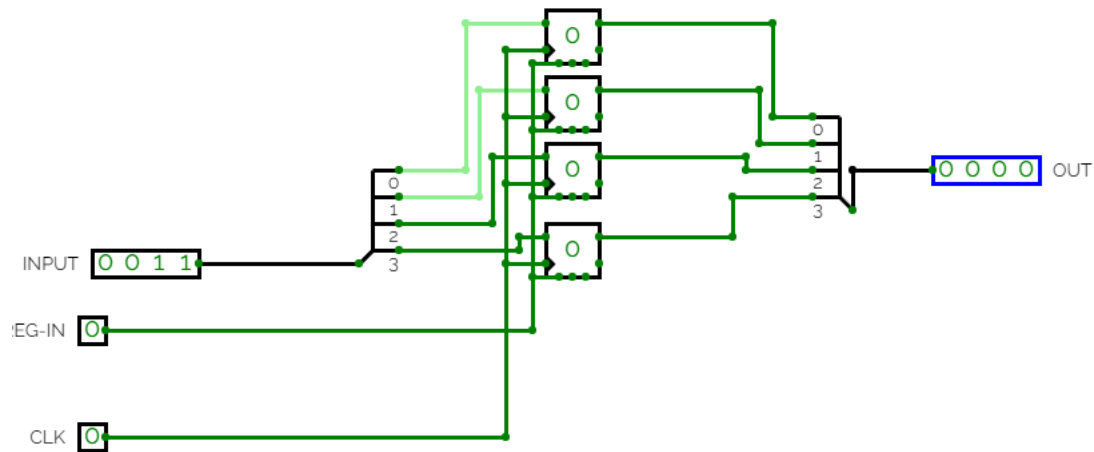


Figure 4: Memory Address Register

### 4.2 MAR\_IN

If  $MAR\_IN = 1$  , then the MAR takes the 4-bit address (Least Significant in common bus) from the Program Counter through common bus.



## 5 INSTRUCTION REGISTER

### 5.1 Diagram

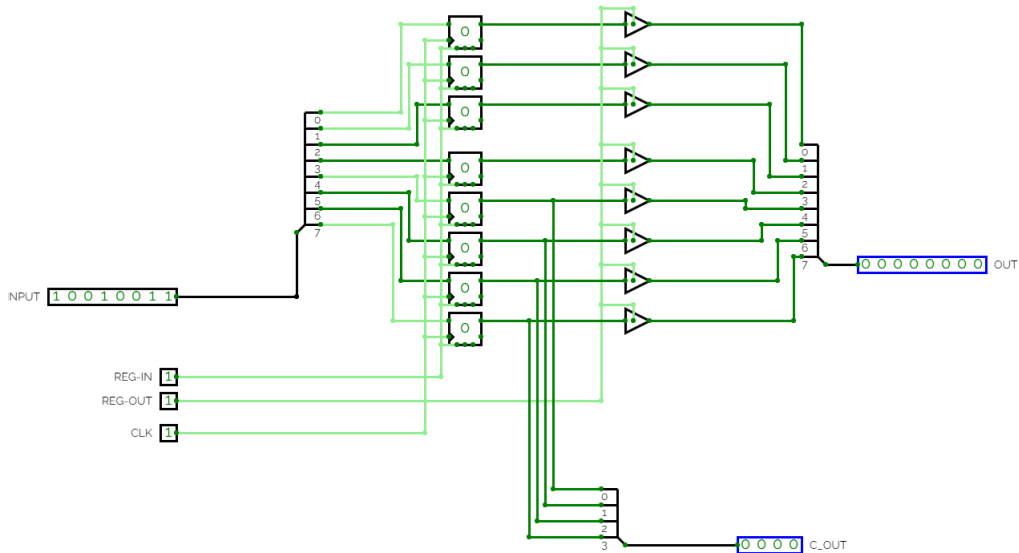


Figure 5: Instruction Register

To fetch an instruction from the memory the computer does a memory read operation . This places the contents of the addressed memory location on the common bus. The instruction register loads this content into it on the next positive clock edge .

The contents of the instruction register are split into two nibbles of 4-bits each (least 4 significant bits , most 4-significant bits) , The most 4-significant bits are sent into **Controller** and it will also send the 8-bit content into the **Instruction decoder** .

The following are the functionalities that are present in the Instruction register .

### 5.2 INS\_REG\_IN

If  $INS\_REG\_IN = 1$  , then the INS register takes the 8-bit content as input from the common bus .

### 5.3 INS\_REG\_OUT

If  $INS\_REG\_OUT = 1$  , then INS register loads its 8-bit content into Instruction decoder and thus into common bus.

### 5.4 CTRL

The Most Significant 4-bits(4-7) load in to the **Controller** and **INS Decoder**.

## 6 INSTRUCTION DECODER

### 6.1 Diagram

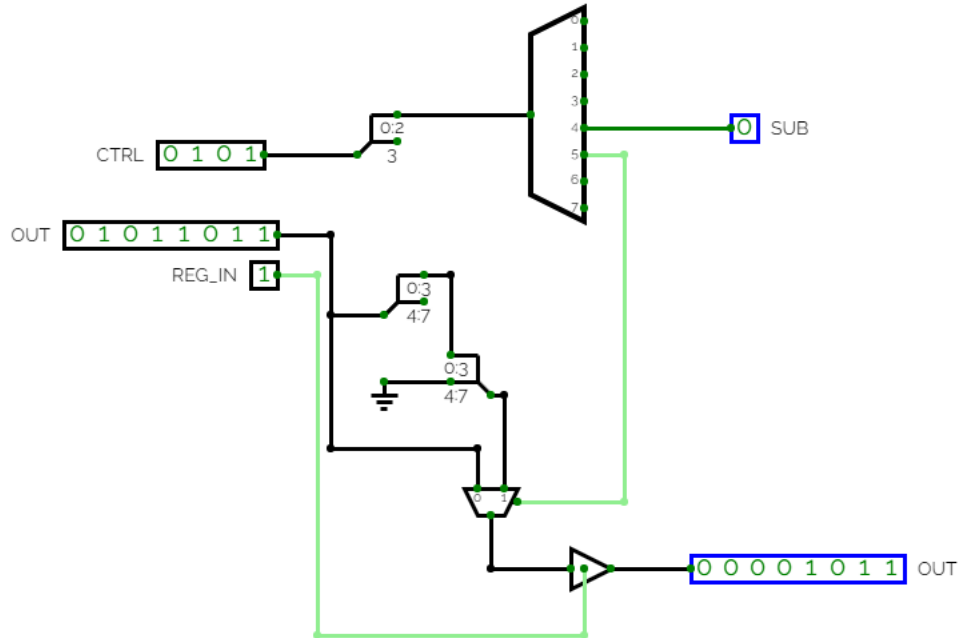


Figure 6: Instruction Decoder

It helps the ALU by giving the instruction whether to add or subtract , by using the most significant 4-bits (i.e CTRL) . It also helps us with the instruction **LDI** by making the 4 - most significant bits into 0000 , so that the remaining 4-bits gets stored in our **accumulator (i.e register A)**.

The following are the functionalities that are present in the Instruction Decoder .

### 6.2 INS \_DEC \_OUT

If  $INS\_DEC\_OUT = 1$  , then it takes the 8-bit content from OUT of INS register .

### 6.3 ALU\_OUT

The  $INS\_DEC$  generates a 1-bit input for the **ALU**.

It generates the following outputs for the corresponding instructions .

$$0 \implies Addition$$

$$1 \implies Subtraction$$

## 7 Arithmetic and Logic Unit(ALU)

 


Figure 7: Gajendra ALU

The ALU performs the arithmetic operations, executed by the computer. Supported operations are Addition(ADD) and Subtraction(SUB). The final 8-bit data is then loaded into Accumulator or REG \_A .

### 7.1 ADD

The ADD operation is used to add two 8-bit numbers using a 8-bit full adder which adds without carry .

### 7.2 SUB

The SUB operation is used to subtract two 8-bit numbers using a 8-bit full adder with initial carry in as 1. This one is supplied by INS\_DEC.

## 8 Status Register

### 8.1 Diagram

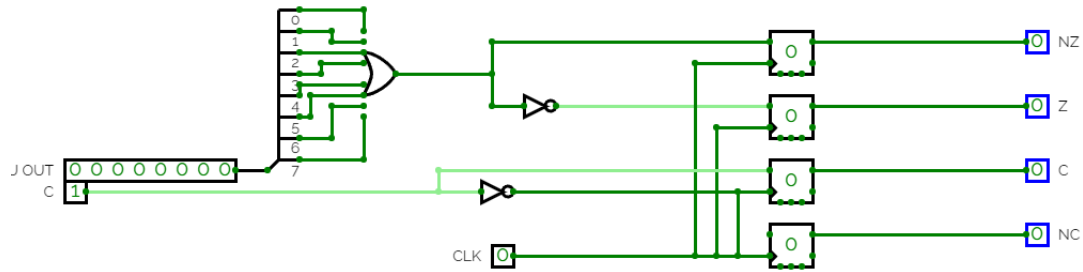


Figure 8: Status Register

### 8.2 I/O

It takes 2 inputs ALU \_OUT and C ( carry out from ALU) and gives four outputs namely: **C** (1 if carry = 1), **NC**( **negation of C**) , **Z**(1 if(**ALU \_OUT** = 1) and **NZ** (**negation of Z**). Tise NZ line is used as input to the controller to aid in the **JNZ** function.

### 8.3 Uses

It is used to implement JUMP and JUMP if not zero conditions.

## 9 Control Processor

### 9.1 Diagram

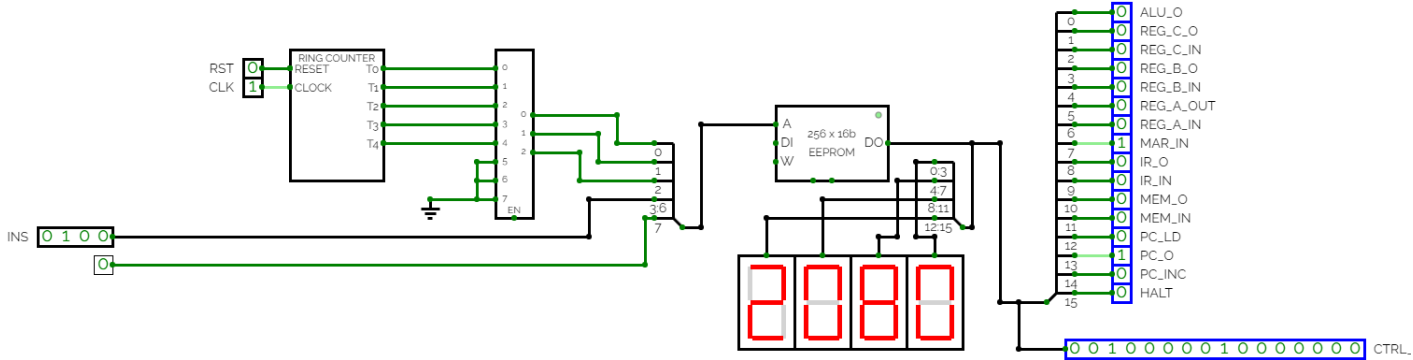


Figure 9: Control Processor

### 9.2 I/O

The control processor takes 4 bit instruction from INS\_REG .We use a ring counter of length 5 indicating the 5 T-states. The EEPROM in the control processor takes 8-bit address is split into 3 parts. The first bit zero and next 4 bits are the instruction and the last 3 bits are the T-state that is to be implemented. The EEPROM gives 16-bit output which is the control word which is also the output of the Control Processor.

### 9.3 Working

The control word consists of all inputs of the program which are: REG\_in, REG\_out, PC\_load, PC\_out, PC\_inc, flag, MEM\_in, MEM\_out, MAR\_in, INS\_out, INS\_out and ALU\_out. It controls all the other components of the program and is hence the most important component of the program .

### 9.4 Ring Counter

Every instruction has micro instructions called 'T states' that are needed to be implemented in a particular sequence one after another. This is done using a ring counter. We use a ring counter of length 5 bits in the program which governs the micro instructions.

### 9.5 EEPROM Programming

Each memory location in EEPROM contains 8 bits necessary to execute its micro instructions. The each memory location contains the control word of that particular micro instruction.

## 10 Micro instructions and Controller Logic Design

### 10.1 NOP :

NOP :	1<<PC_OUT   1<<MAR_IN	T0
	1<<PC_INC   1<<MEM_OUT   1<<IR_IN	T1
	0	T2
	0	T3
	0	T4

Figure 10: Micro Instruction for NOP

### 10.2 LDA :

LDA :	1<<PC_OUT   1<<MAR_IN	T0
	1<<PC_INC   1<<MEM_OUT   1<<IR_IN	T1
	1<<IR_OUT   1<<MAR_IN	T2
	1<<MEM_OUT   1<<REGA_IN	T3
	0	T4

Figure 11: Micro instruction for LDA

### 10.3 ADD :

STA :	1<<PC_OUT   1<<MAR_IN	T0
	1<<PC_INC   1<<MEM_OUT   1<<IR_IN	T1
	1<<MEM_IN   1<<REGA_OUT	T2
	0	T3
	0	T4

Figure 12: Micro instruction for ADD

#### 10.4 SUB :

SUB	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<MAR_IN	T2
	1<<MEM_IN 1<<REGA_OUT	T3
	0	T4

Figure 13: Micro instruction for SUB

#### 10.5 LDI :

LDI	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<REGA_IN	T2
	0	T3
	0	T4

Figure 14: Micro instruction for LDI

#### 10.6 JNZ :

JNZ	:1<<PC_OUT 1<<MAR_IN	T0
	1<<PC_INC 1<<MEM_OUT 1<<IR_IN	T1
	1<<IR_OUT 1<<PC_LOAD	T2
	0	T3
	0	T4

Figure 15: Micro instruction for JNZ